

# YOU'LL FLIP OVER THIS COIN TOSS CIRCUIT

by Jim Stewart



It's Friday night and you're hungry, so you decide to go pick up some food. Maybe a pizza, or maybe some kung-pao chicken. You love them both, but you must choose one or the other. Do you flip a coin? Sure! But now, you can do it electronically! Let's build a coin toss circuit!

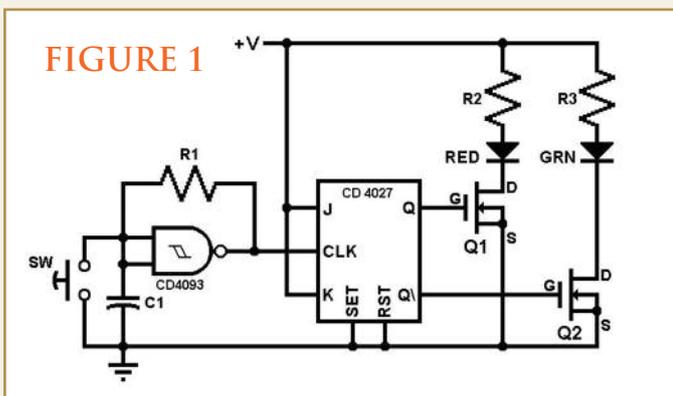


FIGURE 1

## HOW IT WORKS

Figure 1 shows the circuit schematic. It has three sections: a square wave oscillator, a JK flip-flop, and two LEDs (red and green). It uses CMOS digital ICs and MOSFET transistors. The schematic does not show the power and ground connections for the ICs. When powered from a 9V battery, both LEDs will light. When you press the switch, one LED shuts off and the other stays lit; but which one? There's a 50-50 chance for either color.

## OSCILLATOR

The square wave oscillator uses one gate in the CD4093 IC. The IC contains four two-input NAND gates as shown in Figure 2. Digital signals are either high (+V) or low (0V). The output of a gate will switch between high and low, depending on its inputs. The input-output behavior of a gate is defined by its truth table. Table 1 is the truth table for a two-input NAND gate where A and B are the inputs and X is the output. A 0 represents low (0V) while a 1 represents high (+V).

The CD4093 has Schmitt-trigger inputs which means the value of the input voltage required for a 1 depends on whether the input is switching from low to high or from high to low. It's meant to guarantee a "clean" transition on the output but it also allows us to build a simple square wave oscillator.

Suppose the output of the gate is high. Then, current through resistor R1 will charge up capacitor C1 until the input voltage on the gate is high enough to force the output low; call it  $V_a$ . Then, C1 will

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Table 1


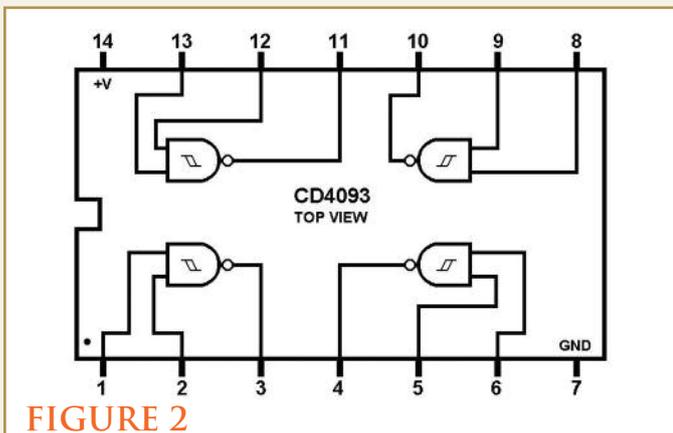


FIGURE 2

discharge through R1, but the switching threshold on the gate has dropped. So, C1 will have to discharge to a voltage lower than  $V_a$ ; call it  $V_b$ . At  $V_b$ , the output will go high but now C1 has to charge back up to  $V_a$ . The process repeats and generates a square wave on the output of the gate. The frequency is determined by the RC time constant  $\tau$ .  $\tau = R1 \times C1$ . Pushing the normally open switch SW shorts the input to ground and stops the oscillation.

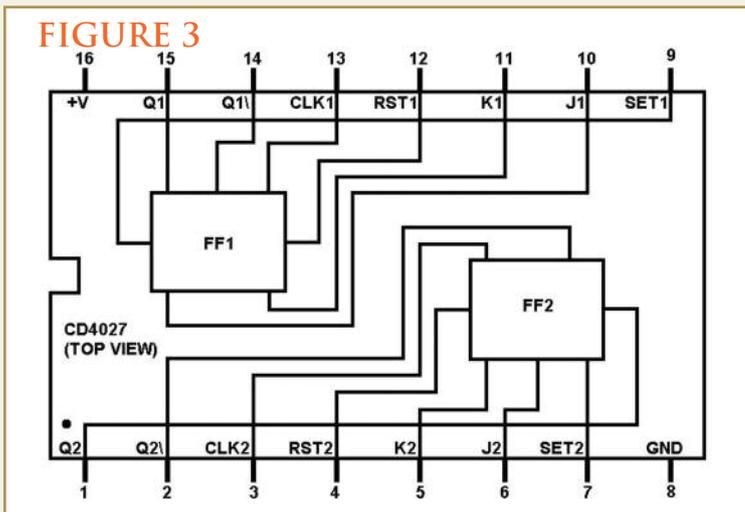

## JK FLIP-FLOP


The CD4027 is a dual JK flip-flop as shown in **Figure 3**. Each flip-flop has three inputs: J, K, and CLK (clock), and two outputs: Q and Q\ (Q\ is read as "Q BAR"). When Q is high, Q\ is low; when Q is low, Q\ is high. The operation of a JK flip-flop is described in **Table 2**. The column  $Q_t$  is the output *before* a clock pulse while the  $Q_{t+1}$  column is the output *after* a clock pulse. The Xs in the table are called "don't cares" meaning they could be 1 (high) or 0 (low).

For this application, the key thing about a JK flip-flop is that when J and K are

J	K	$Q_t$	$Q_{t+1}$
0	0	X	X
0	1	X	0
1	0	X	1
1	1	X	X\

**Table 2**

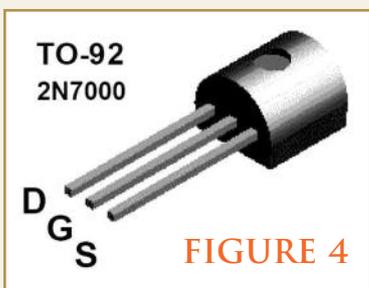both held high, the outputs will toggle each time a pulse is applied to CLK. Toggle means to go to the opposite state. If it was high, it goes low. If it was low, it goes high.





## LEDS AND TRANSISTOR DRIVERS

CMOS logic devices consume little power and will work over a range of voltages (3V-15V). That makes them ideal for battery operation. Unfortunately, you can't get much current from their outputs (~1 mA). The current required to light an LED is 10 mA to 20 mA. To make this work, we will use a pair of MOSFET transistors as drivers for the LEDs. A MOSFET transistor is off until you turn it on by applying +V to the gate (G). Once on, the transistor will conduct up to 200 mA from drain (D) to source (S). **Figure 4** shows the 2N7000 MOSFET transistor.
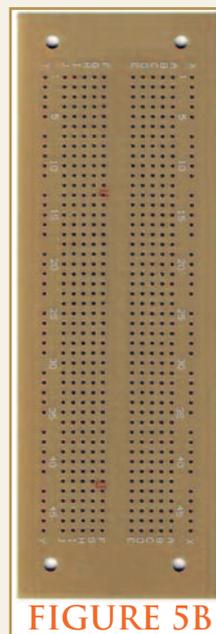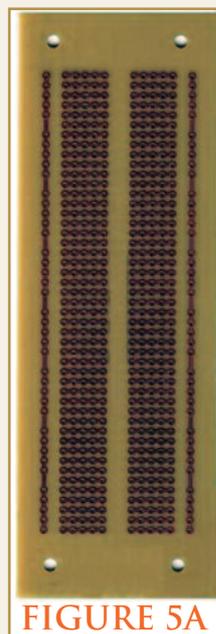
## CIRCUIT BOARD

We will build the circuit on a piece of proto-board as shown in **Figure 5**. The copper side is shown in 5(A) while the component side is shown in 5(B). This style board is ideal for mounting dual inline package (DIP) ICs; you mount them along the middle of the board.

Since we only have two ICs, we don't need the entire proto-board, so I snapped it into two pieces (about a 60-40 split). First, I scored through the copper side cutting the copper and scoring into the phenolic, not cutting all the way through. Once it was scored, I placed the board on the edge of a table with the score line along the edge, copper side up. Holding half the board flat to the table, with a quick motion I pushed the other half down to snap the board. The break wasn't perfectly clean, so I used a file to smooth it out. If all that seems like too much, just use the entire board without snapping it.




## IC SOCKETS AND PARTS LAYOUT

Mistakes happen, and unsoldering an IC is tedious. So, in this project we will use IC sockets. Refer to **Figure 6** to see how the parts are arranged on the board, including jumper wires. **Figure 7** shows how the parts and jumpers are soldered. Note that the leads of the switch need to be adjusted slightly to fit the holes in the board.

## COPPER SIDE

**Figure 7** shows the two strips of copper that run along the top and bottom of the board. They are used for +9V (red wire on battery clip) and ground (black wire). Drill a 1/8 inch hole between the two existing holes. Then, feed the battery clip wires through and make a small knot. Next, feed the black and red wires through the other two holes as shown. In **Figure 6**, you can see the red and black wires inserted into holes and soldered on the copper side. Note the bare wire jumpers, including the one between the two ICs which brings +9V to pins 5 and 6 of the CD4027.

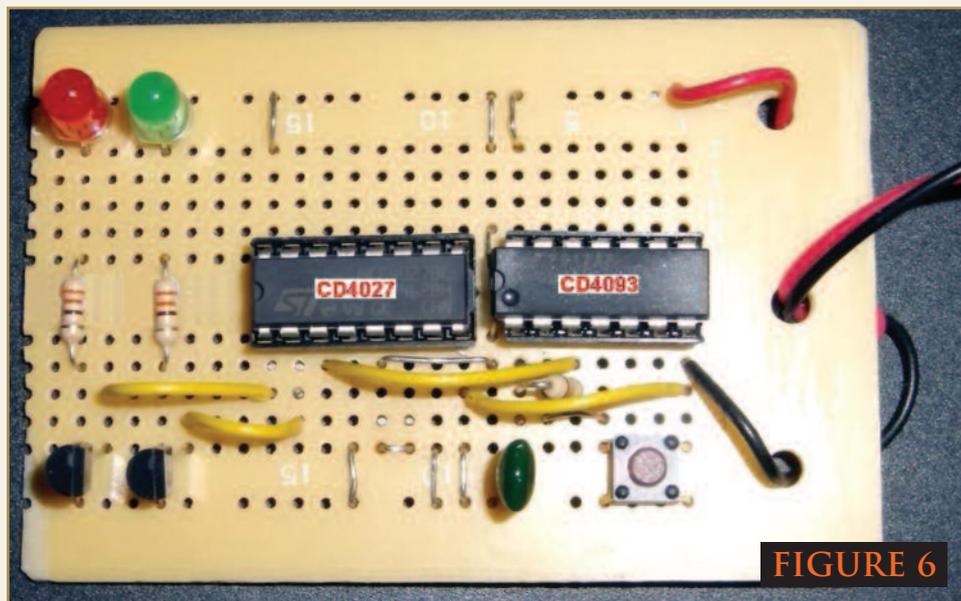

**FIGURE 6**

## WIRING THE SWITCH

Since I cut the board down, it turned out that the switch was connected to the same strips of copper as pins 4 and 7 of the CD4093. So, I had to cut two of the copper traces to isolate the switch from those pins. Be careful to insert the switch correctly. Use an ohmmeter to identify the normally open contacts.

## IC PINS USED


On the CD4093, input pins 1 and 2 and output pin 3 are used for the oscillator; pin 7 is ground and pin 14 is +9V. On the CD4027, pins 1 and 2 are used for Q and Q̄; pin 3 is the input (CLK); pins 4 and 7 (RST and SET) are connected to ground; pins 5 and 6 (K and J) are connected to +9V. Pin 8 is ground and pin 16 is +9V.

## TIME CONSTANT

The exact values of R1 and C1 are not critical. I used 100 kΩ and 0.01 μF to get  $\tau = 1$  ms. Using 0.001 μF for  $\tau = 0.1$  ms would also work. Feel free to play around with the values, but if the time constant gets too big, the LEDs will blink instead of being on steadily.

## FINAL INSPECTION

Insert the ICs into their sockets; be careful to not put them in the wrong way. (You may

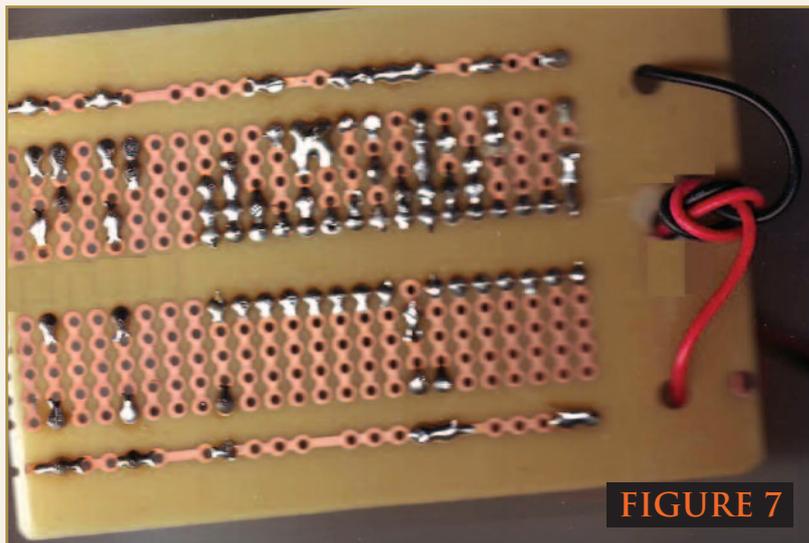

**FIGURE 7**

have to squeeze both sides of an IC to get the pins to go into the socket.) Before applying power, use an ohmmeter to verify there are no shorts between +9V and ground. Verify that the transistors and LEDs are in the right way. Verify that the jumpers connect to the correct points. Look for bad solder joints, missing solder joints, and shorted solder points. Verify that the red and black wires of the battery connector are soldered to the right places.

## TESTING

If it passes final inspection, connect a 9V battery. The two LEDs should immediately light. Press the switch and verify one LED is off and the other is on. Repeat the process several times to verify that the color of the lit LED is red or green at random.

## WRAP UP

Well, that's about it. Have fun with it. Remember to disconnect the battery before putting the circuit away. That's one choice you don't want to flip over. **NV**

### COIN TOSS PARTS LIST

<u>PART</u>	<u>DESCRIPTION</u>	<u>JAMECO PART#</u>
R1	100K, 1/4W, 5%	691340
R2	330W, 1/4W, 5%	690742
R3	330W, 1/4W, 5%	690742
C1	0.01 $\mu$ F Film	26884
IC1	CD4093	13400
IC2	CD4027	12888
Q1	2N7000	783594
Q2	2N7000	783594
SW	Tactile switch (NO)	149948
—	Green LED	1554822
—	Red LED	1554494
—	PROTO-BOARD	616649

[www.jameco.com](http://www.jameco.com)

*Not too long ago, in a  
galaxy not so far away ...  
there was something that  
came along that would change  
the future of robotics forever ...*

**SERVO**  
MAGAZINE

Subscribe **TODAY** and we won't send the Storm Troopers after you!  
Call us at 877-525-2539 or go online at [www.servomagazine.com](http://www.servomagazine.com)